

MODULE 3: Boolean Algebra and Digital Logic

Lecture 3.3 Logic Gates

Prepared By:

- Scott F. Midkiff, PhD
- Luiz A. DaSilva, PhD
- Kendall E. Giles, PhD

Electrical and Computer Engineering
Virginia Tech

Lecture 3.3 Objectives


- Describe the relationship between physical voltage values and logic values of “0” and “1”
- Define the difference between combinational and sequential logic
- Draw the gate symbols associated with the following Boolean operations: AND, OR, NOT, NAND, NOR, XOR, and XNOR
- Derive a gate implementation from an algebraic expression

Physical Realization of Logic Values (1)

- Binary logic values take one of two discrete values
 - “0”(or “LOW” or “FALSE”)
 - “1”(or “HIGH” or “TRUE”)
- While “0” and “1” (or “LOW” and “HIGH” or “TRUE” and “FALSE”) are abstractions, hardware requires physical realization of these values
- The physical world is analog – voltages take on an infinite number of possible values over some continuous range

Physical Realization of Logic Values (2)

 - Digital signals are based on assigned thresholds
- Thresholds to generate logic values are more constrained than thresholds to interpret logic values to avoid ambiguity or errors



(Example thresholds for a common logic family)


Combinational and Sequential Logic

- Consider a logic unit with inputs and outputs (“0” or “1”)
- Outputs of combinational logic depend only on the present values of the inputs
 - The combination of input values completely determines the output values
- Outputs of a sequential logic unit depend on both present input values and past input values, i.e. there is memory



Logic Gates

 
- Logic gates are physical devices that realize simple logic functions
- Symbols are used to represent the fundamental gates Truth tables can be used specify the logic functions



AND Gate

- AND gate implements the AND operation
Output is TRUE (“1”) if and only if all inputs are TRUE (“1”)

a	b	F=ab
0	0	0
0	1	0
1	0	0
1	1	1

 


$$F = a \bullet b = ab$$

OR Gate

- OR gate implements the OR operation
- Output is TRUE (“1”) if and only if at least one or more input is TRUE (“1”)

a	b	$F=a+b$
0	0	0
0	1	1
1	0	1
1	1	1

 

$$F = a+b$$

CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can do the following:


- Write the truth table and the function f , and draw the logic gate symbol for the AND and OR operations.

If you have any difficulties, please review the lecture video before continuing.

NOT Gate (Inverter)

- NOT gate (inverter) implements the NOT operation
- Output is TRUE (“1”) if and only if the input is FALSE (“0”)

a	$F = \bar{a}$
0	1
1	0

 


$$F = a' = \bar{a}$$

NAND Gate

- NAND gate implements the NAND operation – logically merges an AND gate with a NOT gate
- Output is TRUE (“1”) if and only if any input is FALSE (“0”)

a	b	$F = \overline{ab}$
0	0	1
0	1	1
1	0	1
1	1	0

 


$$F = (ab)' = \overline{ab}$$

NOR Gate

- NOR gate implements the NOR operation – logically merges an OR gate with a NOT gate
- Output is TRUE (“1”) if and only if all inputs are FALSE (“0”)

a	b	$F = \overline{a+b}$
0	0	1
0	1	0
1	0	0
1	1	0

 


$$F = (a+b)' = \overline{a+b}$$

Exclusive-OR (XOR) Gate

- Output is TRUE (“1”) if and only if an odd number of inputs are TRUE (“1”)

a	b	$F=a\oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

 


$$F = a\oplus b$$

Exclusive-NOR (XNOR) Gate

- Output is TRUE (“1”) if and only if an even number of inputs are TRUE (“1”)
- The inverse of the XOR gate

a	b	$F=a\ominus b$
0	0	1
0	1	0
1	0	0
1	1	1

 

$$F = (a \oplus b)' = a \ominus b$$

CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can:

- Write the truth table and the function f , and draw the logic gate symbol for the NOT, NAND, NOR, XOR, and XNOR operations.

If you have any difficulties, please review the lecture video before continuing.

Example: Definition of Logic Function

- Consider the following Boolean function

$$F(a,b,c,d) = \overline{a}(bd + b\overline{d}) + \overline{(a + b + d)} + \overline{[b + (\overline{c} + d)]} + \overline{abcd}$$

- F is a function of the four Boolean variables a, b, c, and d
- It includes the three basic logic operations, AND, OR, and NOT
- Function F can also be defined by a truth table


Example: Truth Table (Top Half)

a	b	c	d	bd	bd'	(bd+bd')	a'(bd+bd')	(a+b+d)'	(c'+d)	[b+(c'+d)]'	ab'c'd	F
0	0	0	0	0	0	0	0	1	1	0	0	1
0	0	0	1	0	0	0	0	0	1	0	0	0
0	0	1	0	0	0	0	0	1	0	1	0	1
0	0	1	1	0	0	0	0	0	1	0	0	0
0	1	0	0	0	1	1	1	0	1	0	0	1
0	1	0	1	1	0	1	1	0	1	0	0	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	1	1	0	1	0	0	1

Example: Truth Table (Bottom Half)

a	b	c	d	bd	bd'	(bd+bd')	a'(bd+bd')	(a+b+d)'	(c'+d)	[b+(c'+d)]'	ab'c'd	F
1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	1	0	0	0	0	0	1	0	1	1
1	0	1	0	0	0	0	0	0	0	1	0	1
1	0	1	1	0	0	0	0	0	1	0	0	0
1	1	0	0	0	1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0	0	1	0	0	0
1	1	1	0	0	1	1	0	0	0	0	0	0
1	1	1	1	1	0	1	0	0	1	0	0	0

Example: Initial Gate Implementation

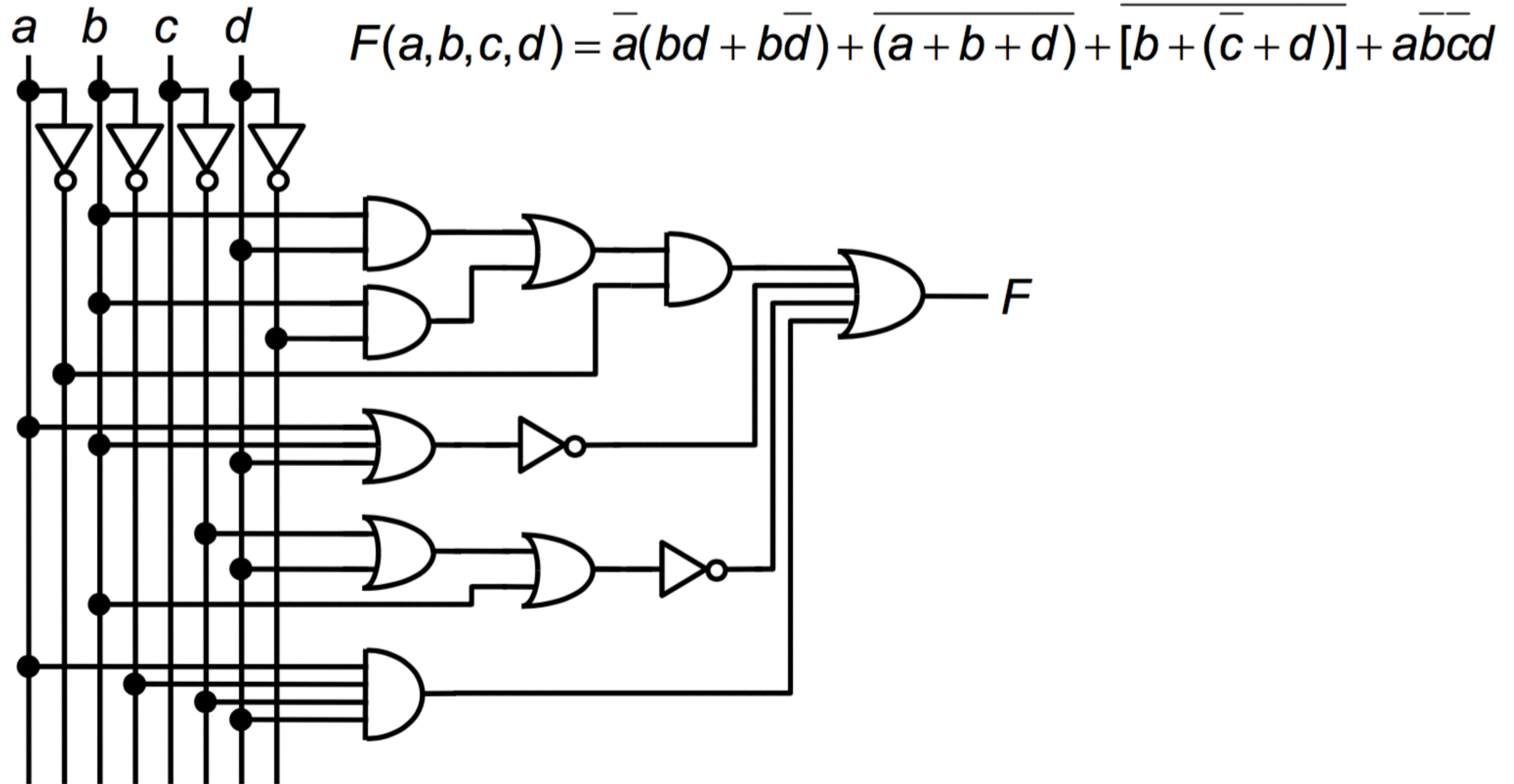

Example: Logic Simplification

- It is sometimes advantageous to realize a Boolean function using a different representation of the same function
 - Reduce number of gates
 - Reduce area for an integrated circuit realization
 - Decrease propagation delay
 - Better match an implementation technology
- Manipulation is usually performed by computer-aided design (CAD) tools for logic design
 - Algebraic manipulation
 - Special algorithms, e.g. the Quine-McCluskey algorithm

Example: Algebraic Simplification

$$\begin{aligned} F(a, b, c, d) &= \bar{a}(bd + b\bar{d}) + \overline{(a + b + d)} + \overline{[b + (\bar{c} + d)]} + a\bar{b}\bar{c}d \\ &= \bar{a}[b(d + \bar{d})] + \overline{(a + b + d)} + \overline{[b + (\bar{c} + d)]} + a\bar{b}\bar{c}d \\ &= \bar{a}[b(1)] + \overline{(a + b + d)} + \overline{[b + (\bar{c} + d)]} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \overline{(a + b + d)} + \overline{[b + (\bar{c} + d)]} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{b}\bar{d} + \overline{[b + (\bar{c} + d)]} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{b}\bar{d} + \bar{b}(\overline{\bar{c} + d}) + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{b}\bar{d} + \bar{b}(\bar{c}\bar{d}) + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{b}\bar{d} + \bar{b}(c\bar{d}) + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{b}\bar{d} + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \end{aligned}$$

Example: Algebraic Simplification (more)

$$\begin{aligned} F(a, b, c, d) &= \bar{a}b + \bar{a}\bar{b}\bar{d} + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \\ &= \bar{a}b(1) + \bar{a}\bar{b}\bar{d} + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \\ &= \bar{a}b(1 + \bar{d}) + \bar{a}\bar{b}\bar{d} + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}b\bar{d} + \bar{a}\bar{b}\bar{d} + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{d}b + \bar{a}\bar{d}\bar{b} + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{d}(b + \bar{b}) + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{d}(1) + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \\ &= \bar{a}b + \bar{a}\bar{d} + \bar{b}c\bar{d} + a\bar{b}\bar{c}d \end{aligned}$$


CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can:

- Work through by hand the steps to simplify the function F on slide 21.

If you have any difficulties, please review the lecture video before continuing.

Simplified Implementation

 

$$F(a,b,c,d) = \bar{a}b + \bar{a}d + bcd + abcd$$

Example: Comparison

- Both logic circuits realize the same Boolean function
- Let's compare the original realization and the new realization

	Inverters	Gates	Longest Path
Original	6	9	5
New	4	5	3


- While an exact comparison depends on the implementation technology, it is likely that the new design requires less area and operates with less delay than the original design

Example: NAND Gate Implementation (1)

- Back to back “invert bubbles” are added between the first-level AND gates and the second-level OR gate
- NAND gates replace each AND and OR gate

$$F(a,b,c,d) = \overline{\overline{a}b} \bullet \overline{\overline{a}d} \bullet \overline{\overline{b}cd} \bullet \overline{ab\overline{c}d}$$

Example: NAND Gate Implementation (2)

 

CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can:

- On slide 24 write by hand the simplified function F and draw its logic gate diagram.

If you have any difficulties, please review the lecture video before continuing.

Summary

- Logic values (“1” and “0”) are abstractions of physical signals with “1” or “0” values based on thresholds for a particular technology
- Combinational logic functions depend only on current inputs; sequential logic functions depend on current and past inputs
- Logic gates implement simple logic operations such as AND, OR, NOT, and NAND
- As an example, we realized a Boolean function using gates and found an alternative realization using algebraic manipulation of the expression

MODULE 3: Boolean Algebra and Digital Logic

Lecture 3.3 Logic Gates

Prepared By:

- Scott F. Midkiff, PhD
- Luiz A. DaSilva, PhD
- Kendall E. Giles, PhD

Electrical and Computer Engineering
Virginia Tech