

Gasser Ahmed
gasser18@vt.edu
 ECE 5484, Project 1

Section 1 – Objectives:

Design a combinational logic circuit that displays the hexadecimal value of a gray code input according to the specifications below:

Hexadecimal Value	Balanced Gray Code ($X_3X_2X_1X_0$)	Binary Code ($Y_3Y_2Y_1Y_0$)
0	0 0 0 0	0 0 0 0
1	1 0 0 0	0 0 0 1
2	1 1 0 0	0 0 1 0
3	1 1 0 1	0 0 1 1
4	1 1 1 1	0 1 0 0
5	1 1 1 0	0 1 0 1
6	1 0 1 0	0 1 1 0
7	0 0 1 0	0 1 1 1
8	0 1 1 0	1 0 0 0
9	0 1 0 0	1 0 0 1
A	0 1 0 1	1 0 1 0
B	0 1 1 1	1 0 1 1
C	0 0 1 1	1 1 0 0
D	1 0 1 1	1 1 0 1
E	1 0 0 1	1 1 1 0
F	0 0 0 1	1 1 1 1

By following the steps below:

1. Create truth table by reordering the table given above.
2. Create SOP Boolean logic expressions for all four outputs Y_0 , Y_1 , Y_2 , and Y_3 from the truth table.
3. Simplify those expressions using K-Maps.
4. Design the circuit layout for the simplified expressions using Digital.
5. Debug and test the full system by observing specified versus actual hexadecimal outputs for different input combinations.

Section 2 – Truth Table:

Hexadecimal Value	Balanced Gray Code (X ₃ X ₂ X ₁ X ₀)	Binary Code (Y ₃ Y ₂ Y ₁ Y ₀)
0	0 0 0 0	0 0 0 0
F	0 0 0 1	1 1 1 1
7	0 0 1 0	0 1 1 1
C	0 0 1 1	1 1 0 0
9	0 1 0 0	1 0 0 1
A	0 1 0 1	1 0 1 0
8	0 1 1 0	1 0 0 0
B	0 1 1 1	1 0 1 1
1	1 0 0 0	0 0 0 1
E	1 0 0 1	1 1 1 0
6	1 0 1 0	0 1 1 0
D	1 0 1 1	1 1 0 1
2	1 1 0 0	0 0 1 0
3	1 1 0 1	0 0 1 1
5	1 1 1 0	0 1 0 1
4	1 1 1 1	0 1 0 0

Section 3 – Logic Expressions:

$$Y_0 = X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3$$

K-Map:

$X_3X_2 \backslash X_1X_0$	X_1X_0	X_1X_0	X_1X_0	X_1X_0
X_3X_2	0	1	0	1
X_3X_2	1	0	1	0
X_3X_2	0	1	0	1
X_3X_2	1	0	1	0

No Reduction

$$Y_1 = X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3$$

K-Map:

$X_3X_2 \backslash X_1X_0$	X_1X_0	X_1X_0	X_1X_0	X_1X_0
X_3X_2	0	1	0	1
X_3X_2	0	1	1	0
X_3X_2	1	1	0	0
X_3X_2	0	1	0	1

After reduction $Y_1 = X_1X_0 + X_2X_1X_0 + X_3X_2X_0 + X_3X_2X_1$

$$Y_2 = X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3$$

K-Map:

$X_3X_2 \backslash X_1X_0$	X_1X_0	X_1X_0	X_1X_0	X_1X_0
X_3X_2	0	1	1	1
X_3X_2	0	0	0	0
X_3X_2	0	0	1	1
X_3X_2	0	1	1	1

After reduction $Y_2 = X_2X_0 + X_2X_1 + X_3X_1$


$$Y_3 = X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3 + X_0X_1X_2X_3$$

K-Map:

$X_3X_2 \backslash X_1X_0$	X_1X_0	X_1X_0	X_1X_0	X_1X_0
X_3X_2	0	1	1	0
X_3X_2	1	1	1	1
X_3X_2	0	0	0	0
X_3X_2	0	1	1	0

After reduction $Y_3 = X_2X_0 + X_3X_2$

Section 4 – Circuit Design:

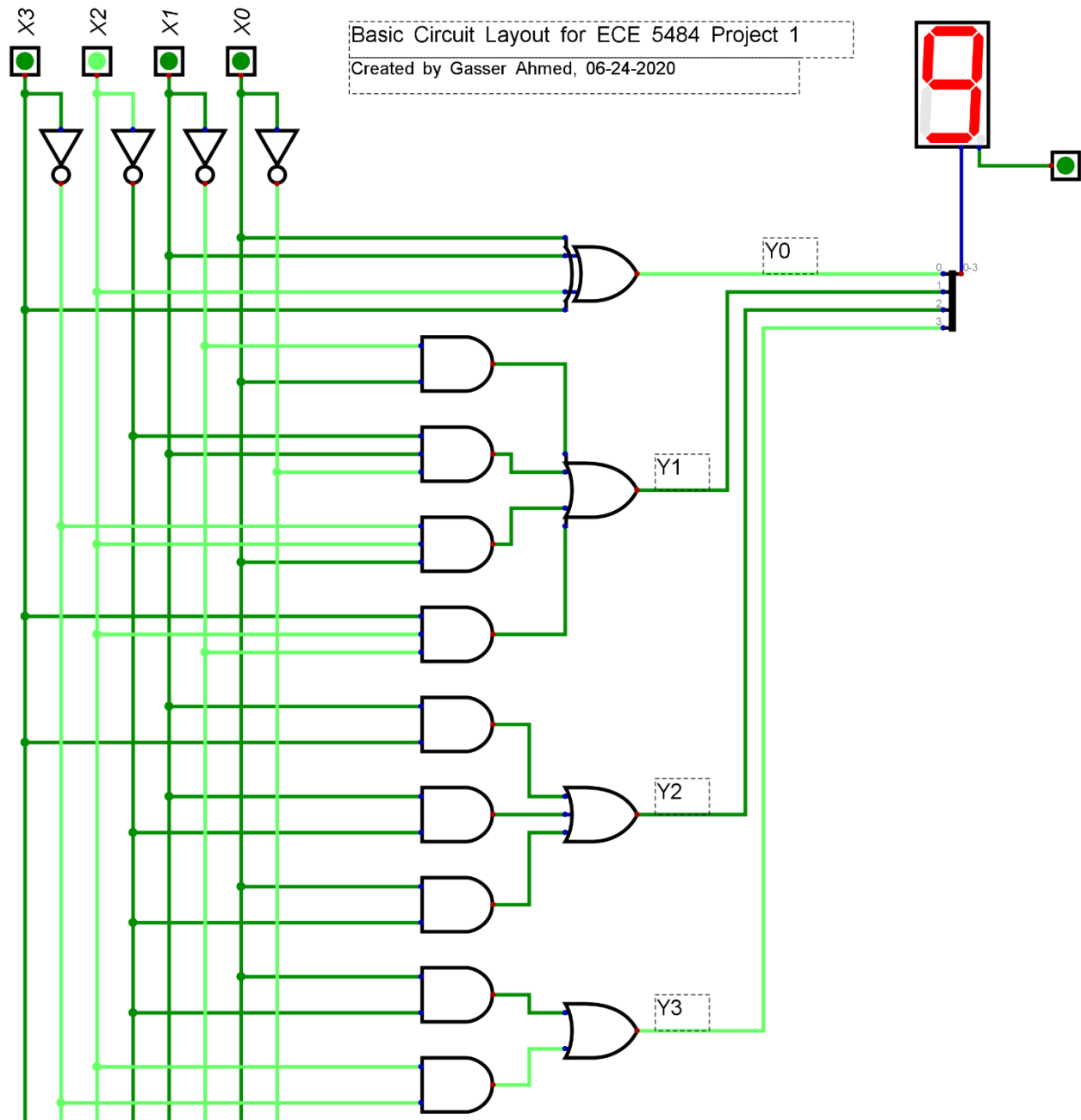

Section 5 – Conclusions:

After designing/simulating the circuit in Digital and testing all different 16 input combinations, I was able to get the correct hexadecimal output for each corresponding input combination. However, in the beginning, I was testing all input combinations, but I was getting wrong outcomes for inputs 1100 and 1110. So, I kept undoing any changes made for the starter circuit for each output Y_1 , Y_2 , and Y_3 until I noticed that those 2 input combinations started to give wrong hexadecimal outcomes when I added the circuit for Y_3 , so I concluded that there should have been something wrong with logic expression for that output Y_3 . So, when I redid the K-Map for Y_3 , I noticed it the current K-Map was wrong compared to the new one which accordingly led to a wrong simplified expression that caused the wrong outcome. Then, after updating the simplified logic expression to match the new K-Map, I tested again all input combinations and I was able to get the correct hexadecimal output for each corresponding input combinations including 1100 and 1110.

So, I learned that testing and debugging all different input combinations is important to make sure the expected outcome is always correct. Also, I learned that I should always doublecheck that I have the correct K-Maps and logical expressions before I start simulating the circuit design in Digital to avoid any conflicts or confusions during testing.

Lastly, the approximate number of hours I devoted to the project was about 8-12 hours. In general, the project was an interesting, learning, and enjoyable experience. Also, the professor's explanations for the project was very helpful and explained a lot of unclear items/objectives.
