

# MODULE 3: Boolean Algebra and Digital Logic

## Lecture 3.6 Flip-Flops

Prepared By:

- Scott F. Midkiff, PhD
- Luiz A. DaSilva, PhD
- Kendall E. Giles, PhD

Electrical and Computer Engineering  
Virginia Tech

# Lecture 3.6 Objectives


- Describe the operation of the unlocked S-R flip-flop and the clocked S-R, J-K, and D flip-flops
- Describe the need for a clock signal in a flip-flop

# Flip-Flops

- Flip-flops are relatively simple circuits that store one bit of information
- The output (the state) depends on the current inputs and the current state
- A flip-flop is a sequential circuit
- Common types of flip-flops
  - S-R (set-reset)
  - J-K
  - D (data)

 
# Block Diagram of an S-R Flip-Flop

- Unclocked (asynchronous) version of the S-R flip-flop
- Inputs S (SET) and R (RESET)
- Output Q (and Q') that depends on present and past inputs of S and R



 
# S-R Flip-Flop (1)

- One form of an S-R flip-flop is built from “cross-coupled” NOR gates


 
# S-R Flip-Flop (2)

- Redrawing the gate-level diagram reveals that there is one “feedback” path that returns an output back to an input
- This path provides 1 bit of memory



1 feedback path  $\Rightarrow$  storage of 1 bit of information

# CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can do the following:


- Draw the block diagram of an unclocked S-R flip-flop, including labeling the inputs and outputs

If you have any difficulties, please review the lecture video before continuing.


 
# Analyzing the S-R Flip-Flop (1)


- Start with the case of  $S=0$ ,  $R=0$ ,  $Q=0$ 
  - Output of  $Q$  stays at 0
  - This is a stable state
- Change  $S$  to 1, so  $S=1$ ,  $R=0$ 
  - $S$  changing to 1 causes  $Q'$  to change from 1 to 0
  - $Q'$  changing from 1 to 0 causes  $Q$  to change from 0 to 1
- $S=1$ ,  $R=0$  “sets” the state (“set” means setting  $Q=1$ )




 
# Analyzing the S-R Flip-Flop (2)

- Continue with the case where the state Q is set,  $S=1$ ,  $R=0$ ,  $Q=1$ 
  - This is a stable state
- Now, change S from 1 back to 0, so  $S=0$ ,  $R=0$ 
  - $Q'$  stays at 0 since  $Q=1$
  - $Q$  stays at 1 since  $Q'=0$ ,  $R=0$
- $S=0$ ,  $R=0$  “holds” the present state



# Analyzing the S-R Flip-Flop (3)

- Further analysis shows that:
  - $S=0, R=1$  “resets” the state, i.e. resets  $Q$  to 0, regardless of the original state of  $Q$
  - $S=1, R=1$  leads to indeterminate results and is, thus, an invalid or forbidden input to the S-R flip-flop

# Analyzing the S-R Flip-Flop (4)

- The S-R flip-flop provides memory for one state bit
  - We can store “1” by doing a SET ( $S=1, R=0$ )
  - We can store “0” by doing a RESET ( $S=0, R=1$ )
  - We can hold the present state by doing a HOLD ( $S=0, R=0$ )
- This or similar circuits are the basis for other sequential logic elements such as clocked flip-flops and static random access memory (SRAM)


# State (Truth) Table for the S-R Flip-Flop

- Specifies value of  $Q_{t+1}$  as a function of S, R, and  $Q_t$ 
  - $Q_t$  is the present state of state bit Q
  - $Q_{t+1}$  is the next state of state bit Q
- Three operations
  - Hold (Q does not change)
  - Reset (Q is reset to 0)
  - Set (Q is set to 1)
- Input S=1, R=1 is invalid

	S	R	$Q_t$	$Q_{t+1}$
HOLD	0	0	0	0
	0	0	1	1
RESET	0	1	0	0
	0	1	1	0
SET	1	0	0	1
	1	0	1	1
invalid	1	1	0	—
	1	1	1	—
 
# State Transition Diagram for S-R F-F

- Two nodes, for  $Q=0$  and  $Q=1$
- Edges labeled with values of  $SR$  that cause the indicated transition
- For example, analysis showed that  $SR=10$  with  $Q=0$  caused a state change to  $Q=1$ 
  - This transition corresponds to one edge in the graph





# CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can do the following:

- Describe the operation of the unclocked S-R flip-flop using a state-transition diagram

If you have any difficulties, please review the lecture video before continuing.


# Glitches and Unclocked Flip-Flops (1)

- Spurious, short transitions (glitches) can occur on the output of combinational logic units
  - Such glitches are due to differences in propagation delays through the logic circuit when one or more inputs changes its value
  - A circuit has a “hazard” if it can produce a glitch at its output
- A glitch can cause problems for an unclocked (asynchronous) sequential circuit



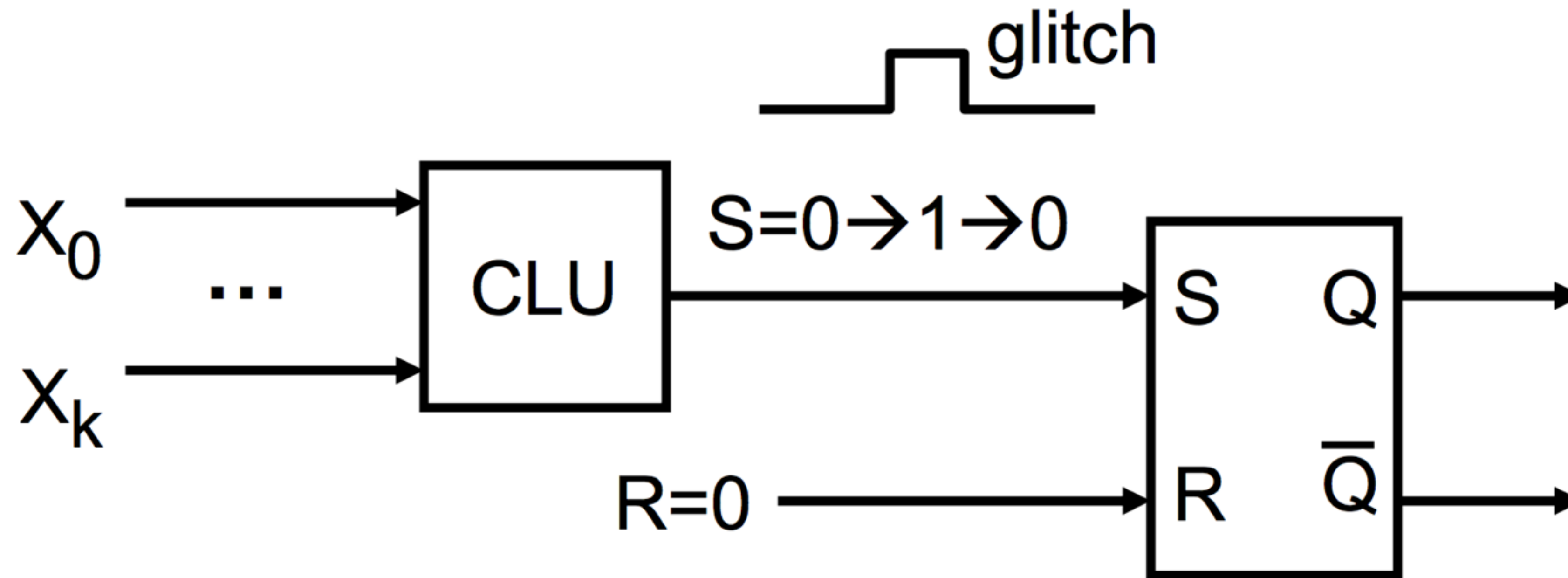
# Glitches and Unclocked Flip-Flops (2)

- Consider a combinational logic unit (CLU) that drives the S input on an unclocked S-R flip-flop
- A glitch on input S can cause an unintended transition in Q



# Glitches and Unclocked Flip-Flops (3)

 



- The unexpected glitch in S causes an unexpected SET operation to be performed, causing Q to go to 1 when we want it to stay (since  $S=0$ ,  $R=0$ )

# Clocked Flip-Flops (1)

- A solution to the problems of such glitches is to use a clock to create a “synchronous” sequential circuit
- Clock events cause the flip-flop to sample the inputs and to use the sampled values to determine a change in the output

  
# Clocked Flip-Flops (2)

- Output only changes due to a clock event
  - Rising (0-to-1) clock edge: positive edge-triggered flip-flop
  - Falling (1-to-0) clock edge: negative edge-triggered flip-flop
  - High clock: level triggered


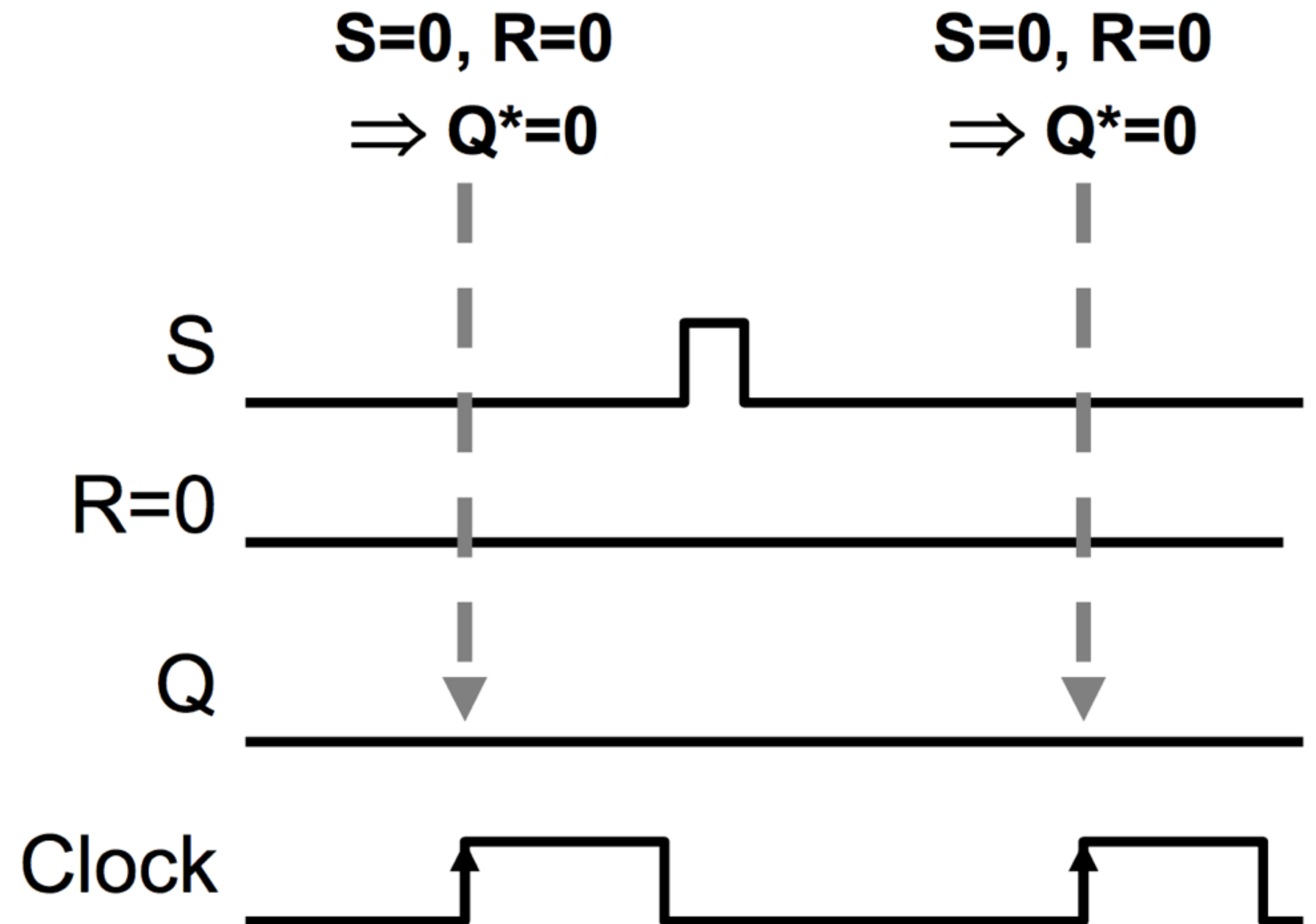
# Clocking to Avoid Glitches

- Rising edge in clock determines when the S-R flip-flop changes its state
- Operates as expected as glitch is between rising edges of the clock and is ignored



# CHECK POINT



As a checkpoint of your understanding, please pause the video and make sure you can do the following:

- Use input and output signal timelines to describe how clocking helps avoid glitches in the operation of the S-R flip-flop

If you have any difficulties, please review the lecture video before continuing.



# Block Diagrams for Clocked S-R F-F

  



# Clocking

- The clock must be properly designed
  - Slow enough to ensure that all flip-flop inputs are stable before the next clock event occurs
  - Fast enough to provide fast circuit operation (desirable for most designs)

# Other Flip-Flops


- The clocked S-R flip-flop can be used as a basis for other types of clocked flip-flops, including:
  - D or “Data” flip-flop
  - J-K flip-flop (modified S-R flip-flop function)
- We assume clocked, edge-triggered flip-flops

# “Data” or D Flip-Flop

- The D flip-flop simply stores the D input (0 or 1) that is present at each clock event
- Can be built using an S-R flip-flop
  - If  $D=1$ , then  $S=1$  and  $R=0$  for a SET operation ( $Q=1$ )
  - If  $D=0$ , then  $S=0$  and  $R=1$  for a RESET operation ( $Q=0$ )


State Table

D	$Q_t$	$Q_{t+1}$
0	0	0
0	1	0
1	0	1
1	1	1

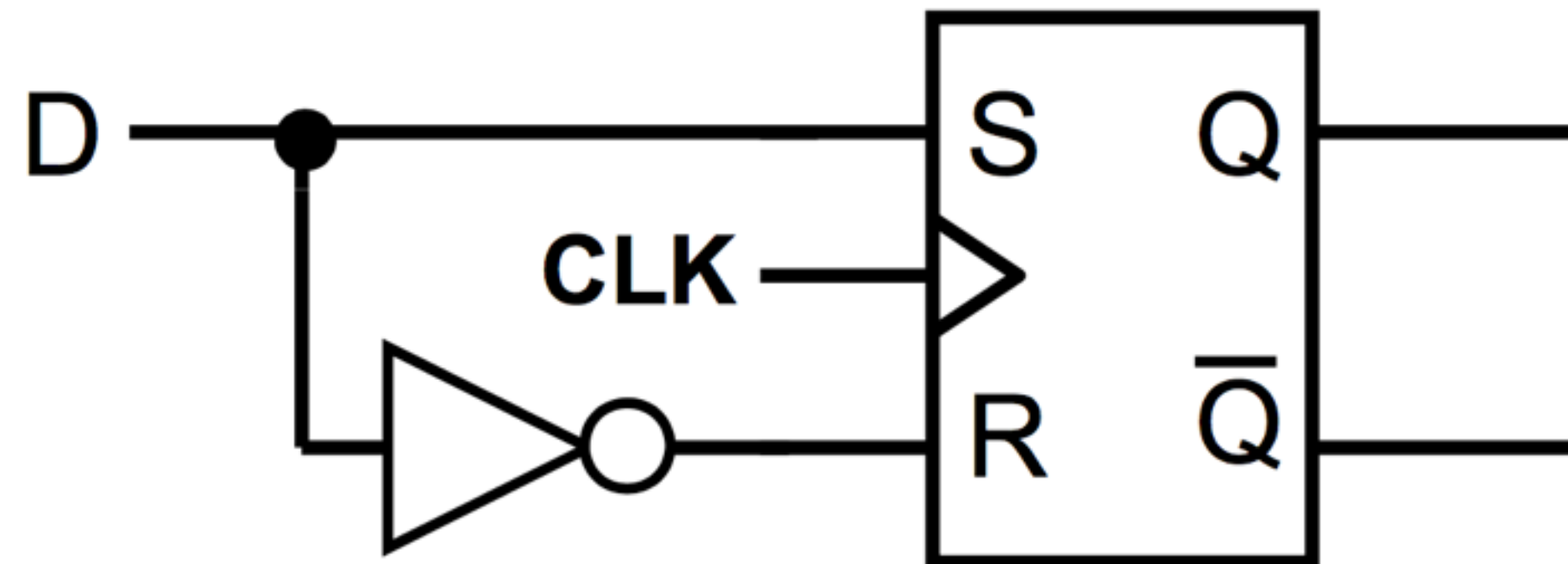
 
# D Flip-Flop Operation

- Output Q takes on the value of D present at each positive clock edge
- For example:
- At (2), D=1, so Q changes from 0 to 1
- At( 3), D=0, so Q changes from 1 to 0
- Value of D=1 between (3) and (4) is ignored since not clocked




# J-K Flip-Flop

- J-K flip-flop is like an S-R flip-flop (with  $J=S$  and  $K=R$ ) except for the case where inputs are both 1
- $S=1$ ,  $R=1$  not allowed for the S-R flip-flop
- $J=1$ ,  $K=1$  is allowed and causes the state to toggle
- $Q=0$  toggles to  $Q=1$
- $Q=1$  toggles to  $Q=0$

	J	K	$Q_t$	$Q_{t+1}$
HOLD	0	0	0	0
	0	0	1	1
RESET	0	1	0	0
	0	1	1	0
SET	1	0	0	1
	1	0	1	1
TOGGLE	1	1	0	1
	1	1	1	0
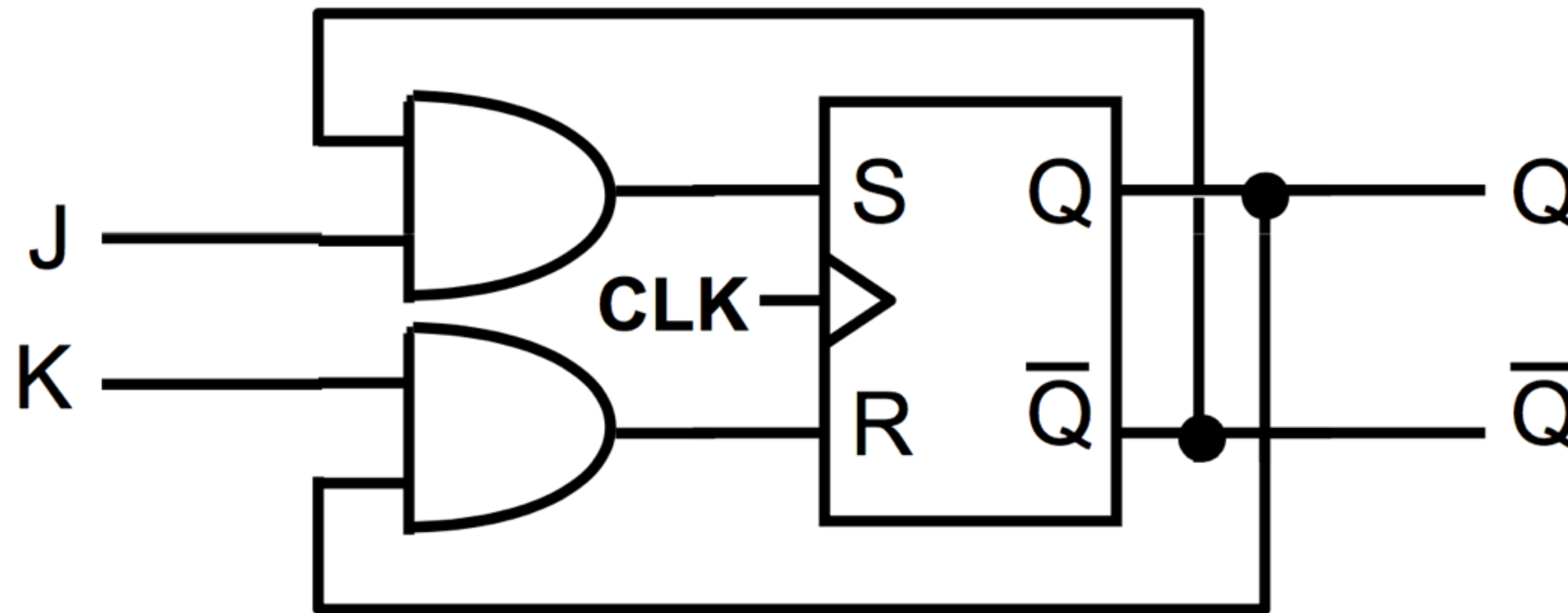
# J-K Flip-Flop Logic

- Logic implements  $S = JQ'$  and  $R = KQ$
- Example: Assume  $J = K = 1$  (TOGGLE operation)
- If  $Q = 0$ , then  $S = 1$ ,  $R = 0$  (to SET) and next state is  $Q = 1$
- If  $Q = 1$ , then  $S = 0$ ,  $R = 1$  (to RESET) and next state is  $Q = 0$





# CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can do the following:

- Use a state table to describe the operation of a D flip-flop
- Draw the J-K flip-flop logic circuit using the block diagram of a clocked S-R flip-flop and two AND gates

If you have any difficulties, please review the lecture video before continuing.



# Summary (1)

- S-R flip-flop constructed from two NOR gates (or two NAND gates)
  - Analyzed logic circuit to determine behavior
  - Specified behavior using a state table and state transition diagram
- Glitches create problems for unclocked flip-flops, but are not a problem for valid designs using clocked flip-flops
- Clocked flip-flops only change state when a clock event occurs, e.g., a negative edge in the clock signal

# Summary (2)

- Common types of flip-flops
  - S-R flip-flop
  - J-K flip-flop
  - D flip-flop
- Some variations
  - Negative and positive edge-triggered
  - Asynchronous PRESET and CLEAR initialization input signals
- J-K and D flip-flops can be implemented using an S-R flip-flop and some additional combinational logic

# MODULE 3: Boolean Algebra and Digital Logic

## Lecture 3.6 Flip-Flops

Prepared By:

- Scott F. Midkiff, PhD
- Luiz A. DaSilva, PhD
- Kendall E. Giles, PhD

Electrical and Computer Engineering  
Virginia Tech