

MODULE 3: Boolean Algebra and Digital Logic

Lecture 3.2

Representing Boolean Functions

Prepared By:

- Scott F. Midkiff, PhD
- Luiz A. DaSilva, PhD
- Kendall E. Giles, PhD

Electrical and Computer Engineering
Virginia Tech

Lecture 3.2 Objectives

- Represent Boolean functions in sum-of-product (SOP) form
- Represent Boolean functions in product-of-sum (POS) form
- Define “minterm” and “maxterm”

Example Logic Function and Minterms

- Consider function $f(a,b,c)$ specified by the truth table below
- Every row in the truth table corresponds to a unique combination of values for inputs a , b , and c
- Every row corresponds to a “minterm” containing all variables

| a | b | c | f | minterm |
|----------|----------|----------|----------|----------------|
| 0 | 0 | 0 | 1 | $a'b'c'$ |
| 0 | 0 | 1 | 1 | $a'b'c$ |
| 0 | 1 | 0 | 0 | $a'bc'$ |
| 0 | 1 | 1 | 1 | $a'bc$ |
| 1 | 0 | 0 | 1 | $ab'c'$ |
| 1 | 0 | 1 | 0 | $ab'c$ |
| 1 | 1 | 0 | 0 | abc' |
| 1 | 1 | 1 | 1 | abc |

More on Minterms

- Example function $f(a,b,c)$ is TRUE (“1”) if and only if the minterm in each row with $f=1$ is TRUE
- For example, $f = 1$ if $ab'c' = 1$, i.e., $a=1, b=0, c=0$

| a | b | c | f | minterm |
|----------|----------|----------|----------|----------------------------|
| 0 | 0 | 0 | 1 | $a'b'c'$ |
| 0 | 0 | 1 | 1 | $a'b'c$ |
| 0 | 1 | 0 | 0 | $a'bc'$ |
| 0 | 1 | 1 | 1 | $a'bc$ |
| 1 | 0 | 0 | 1 | $ab'c'$ |
| 1 | 0 | 1 | 0 | $ab'c$ |
| 1 | 1 | 0 | 0 | abc' |
| 1 | 1 | 1 | 1 | abc |

Sum-of-Product (SOP) Form

- Example function $f(a,b,c)$ can be expressed as the “OR” of the true minterms
- $f(a,b,c) = a'b'c' + a'b'c + a'bc + ab'c' + abc$
- This is the canonical sum-of-products form of function f , using two-level AND/OR logic

| a | b | c | f | minterm |
|----------|----------|----------|----------|----------------------------|
| 0 | 0 | 0 | 1 | $a'b'c'$ |
| 0 | 0 | 1 | 1 | $a'b'c$ |
| 0 | 1 | 0 | 0 | $a'bc'$ |
| 0 | 1 | 1 | 1 | $a'bc$ |
| 1 | 0 | 0 | 1 | $ab'c'$ |
| 1 | 0 | 1 | 0 | $ab'c$ |
| 1 | 1 | 0 | 0 | abc' |
| 1 | 1 | 1 | 1 | abc |

NAND Function

- NAND function is realized by applying AND and then NOT Output is TRUE (“1”) if and only if any input is FALSE (“0”)

| a | b | $F = \overline{ab}$ |
|---|---|---------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

$$F = (ab)' = \overline{ab}$$

NAND/NAND Form

- Example function $f(a,b,c)$ can also be implemented in NAND/NAND form using DeMorgan's Theorem, $(x+y)' = x'y'$
- So, $f(a,b,c)$ can be realized using AND and OR operations or using only NAND operations

$$\text{Step 1: } f = a'b'c' + a'b'c + a'bc + ab'c' + abc$$

$$\text{Step 2: } f = [(a'b'c' + a'b'c + a'bc + ab'c' + abc)']'$$

$$\text{Step 3: } f = [(a'b'c')' (a'b'c)' (a'bc)' (ab'c')' (abc)']'$$

CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can do the following:

- For the truth table on slide 3, by hand write the AND/OR sum-of-product form of function f , then convert that function into the NAND/NAND form.

If you have any difficulties, please review the lecture video before continuing.

f' , Inverse of Function f

- Consider the inverse of example function $f(a,b,c)$
- We can determine the SOP form of function f'
 - $f(a,b,c)' = a'bc' + ab'c + abc'$

| | a | b | c | f | f' | minterm |
|---------------|----------|----------|----------|----------|-----------|----------------------------|
| | 0 | 0 | 0 | 1 | 0 | $a'b'c'$ |
| | 0 | 0 | 1 | 1 | 0 | $a'b'c$ |
| \Rightarrow | 0 | 1 | 0 | 0 | 1 | $a'bc'$ |
| | 0 | 1 | 1 | 1 | 0 | $a'bc$ |
| | 1 | 0 | 0 | 1 | 0 | $ab'c'$ |
| \Rightarrow | 1 | 0 | 1 | 0 | 1 | $ab'c$ |
| \Rightarrow | 1 | 1 | 0 | 0 | 1 | abc' |
| | 1 | 1 | 1 | 1 | 0 | abc |

Product-of-Sums (POS) Form

- Function f' can be manipulated to yield the product-of-sums form for function f using OR and AND operations

$$\text{Step 1: } f' = a'bc' + ab'c + abc'$$

$$\text{Step 2: } f = (a'bc' + ab'c + abc')'$$

$$\text{Step 3: } f = (a'bc')' (ab'c)' (abc')'$$

$$\text{Step 4: } f = (a''+b'+c'') (a'+b''+c') (a'+b'+c'')$$

$$\text{Step 5: } f = (a+b'+c) (a'+b+c') (a'+b'+c)$$

Canonical POS Form (1)

- A “maxterm” can be associated with each row of the truth table
- Maxterm is an OR expression
- Maxterm is FALSE for the input combination, but TRUE for all others

| | a | b | c | f | maxterm |
|---------------|----------|----------|----------|----------|------------------------------|
| | 0 | 0 | 0 | 1 | $a+b+c$ |
| | 0 | 0 | 1 | 1 | $a+b+c'$ |
| \Rightarrow | 0 | 1 | 0 | 0 | $a+b'+c$ |
| | 0 | 1 | 1 | 1 | $a+b'+c'$ |
| | 1 | 0 | 0 | 1 | $a'+b+c$ |
| \Rightarrow | 1 | 0 | 1 | 0 | $a'+b+c'$ |
| \Rightarrow | 1 | 1 | 0 | 0 | $a'+b'+c$ |
| | 1 | 1 | 1 | 1 | $a'+b'+c'$ |

Canonical POS Form (2)

- Function $f(a,b,c)$ can be written as the product of the maxterms where $f = 0$
 - $f = (a+b'+c)(a'+b+c')(a'+b'+c)$
 - This is the canonical product-of-sums form

| | a | b | c | f | maxterm |
|---------------|----------|----------|----------|----------|------------------------------|
| | 0 | 0 | 0 | 1 | $a+b+c$ |
| | 0 | 0 | 1 | 1 | $a+b+c'$ |
| \Rightarrow | 0 | 1 | 0 | 0 | $a+b'+c$ |
| | 0 | 1 | 1 | 1 | $a+b'+c'$ |
| | 1 | 0 | 0 | 1 | $a'+b+c$ |
| \Rightarrow | 1 | 0 | 1 | 0 | $a'+b+c'$ |
| \Rightarrow | 1 | 1 | 0 | 0 | $a'+b'+c$ |
| | 1 | 1 | 1 | 1 | $a'+b'+c'$ |

NOR Operation

- NOR function is realized by applying OR and then NOT
- Output is TRUE (“1”) if and only if all inputs are FALSE (“0”)

| a | b | $F = \overline{a+b}$ |
|---|---|----------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

$$F = (a+b)' = \overline{a+b}$$

NOR/NOR Form

- Example function $f(a,b,c)$ can also be implemented in NOR/NOR form using DeMorgan's Theorem, $(xy)' = x' + y'$
- So, $f(a,b,c)$ can be realized using only NOR operations

$$\text{Step 1: } f = (a + b' + c) (a' + b + c') (a' + b' + c)$$

$$\text{Step 2: } f = \{ [(a + b' + c) (a' + b + c') (a' + b' + c)]' \}'$$

$$\text{Step 3: } f = \{ (a + b' + c)' + (a' + b + c')' + (a' + b' + c)' \}'$$

CHECK POINT

As a checkpoint of your understanding, please pause the video and make sure you can:

- On slide 10 write out by hand the function f in sum-of-product form, then work through the steps to convert f into the product-of-sums form, then work through the steps to represent f in the NOR/NOR form.

If you have any difficulties, please review the lecture video before continuing.

Summary

- Any logic expression can be represented and implemented as a two-level logic function
- Two basic forms of representation based on OR and AND operations
 - Sum-of-products: AND/OR
 - Product-of-sums: OR/AND
- Alternate forms based on NAND gates or on NOR operations
 - Sum-of-products: NAND/NAND
 - Product-of-sums: NOR/NOR

MODULE 3: Boolean Algebra and Digital Logic

Lecture 3.2

Representing Boolean Functions

Prepared By:

- Scott F. Midkiff, PhD
- Luiz A. DaSilva, PhD
- Kendall E. Giles, PhD

Electrical and Computer Engineering
Virginia Tech